



Department of Computer Science and Information Engineering

National Cheng Kung University

數位系統實驗

陳培殷老師

國立成功大學 資訊工程系

Digital Integrated Circuit Design Laboratory





...
*Cheng
Kung
Univer
sity*

LAB - 03

陳培殷老師
國立成功大學 資訊工程系

*Di
git
al
In
te
gr
at*



Lab I -- Constant Multiplier (1/3)

最高有效位元
MSB

- There is a 2-bit input X (represented as X1 and X0). A constant multiplier is designed to multiply the input by 3. Finally, show the result with decimal format (0, 1, 2,,9) on Digital Display in the breadboard.

Hint-1:


The output digital number is 0, 3, 6 or 9, respectively, for four different inputs (0, 1, 2, 3).

Input			$\times 3$	
	binary	decimal		
{	00	0	\longrightarrow	0
	01	1		3
	10	2		6
	11	3		9

Lab I -- Constant Multiplier (2/3)

Hint-2:

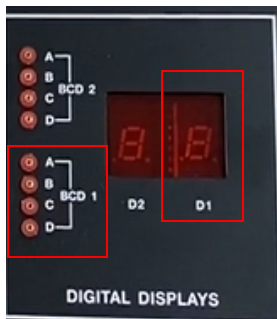Function of the Digital Display in the breadboard is as follows.



D	C	B	A	DIGITAL DISPLAY
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

Lab I -- Constant Multiplier (3/3)


Please




- (a) draw the truth table of the constant multiplier where two input bits are X_1 and X_0 , and four output bits are A, B, C and D, respectively.
- (b) simplify the circuit with K-map (SOP format) and draw the simplified circuit diagram of the constant multiplier.
- (c) implement the circuit on the breadboard.

(a)

X_1	X_0		D	C	B	A
0	0	0	0	0	0	0
0	1	1	3	0	0	1
1	0	2	6	0	1	0
1	1	3	9	1	0	0

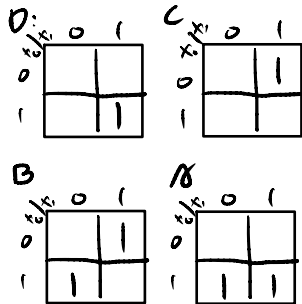$D = X_1 X_0$
 $C = X_1 X_0'$
 $B = X_1 X_0' + X_1' X_0$
 $A = X_0$



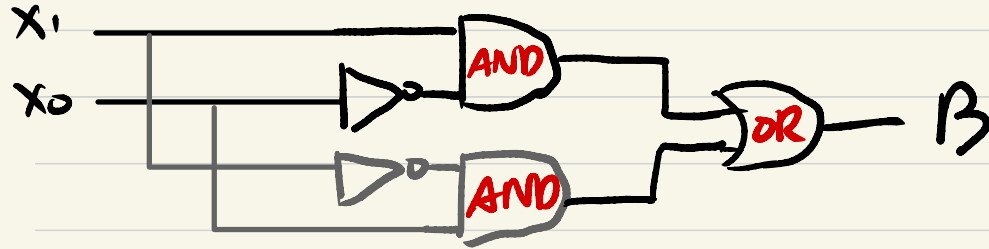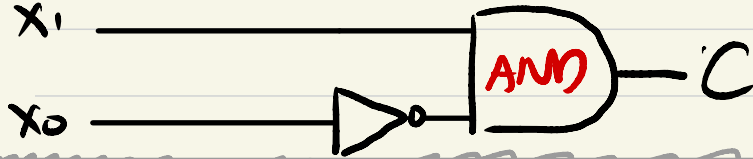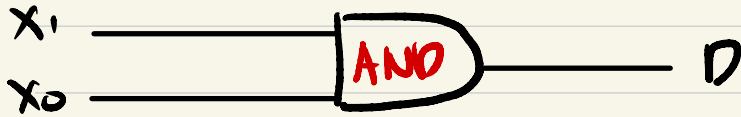

Components needed for LAB I

Names	Amount
Solderless Breadboard	×1
74LS04 NOT	×1
74LS08 AND	×1
74LS32 OR	×1

Lab II – Comparator(1/2)

- There are a 3-bit input X (represented as ^{MSB}X₂, X₁ and ^{LSB}X₀) and two 1-bit outputs A and B. The comparator is designed to let output A be 1 if X>3 and output B be 1 if X>4.
- The function of the comparator is described as follows.

$$A = \begin{cases} 1 & , \text{if } X \text{ is } > 3 \\ 0 & , \text{else} \end{cases}$$

$$B = \begin{cases} 1 & , \text{if } X \text{ is } > 4 \\ 0 & , \text{else} \end{cases}$$

Lab II – Comparator(2/2)

Please

- (a) draw the truth table of the comparator where three input bits are X_2 , X_1 and X_0 , and two output bits are A and B, respectively.
 - (b) simplify the circuit with K-map and draw the simplified SOP-format circuit diagram of the constant multiplier. Finally, implement the circuit on the breadboard.
 - (c) repeat (b) by using the POS format.
-

SOP

X_2	X_1	X_0		A	B
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	2	0	0
0	1	1	3	0	0
1	0	0	4	1	0
1	0	1	5	1	1
1	1	0	6	1	1
1	1	1	7	1	1

A:

X_1, X_0	00	01	11	10
X_2				
0				
1	1	1	1	1


$$A = X_2$$

$$X_2 \text{ ————— } A$$

B:

X_1, X_0	00	01	11	10
X_2				
0				
1		1	1	1

$$B = X_2 X_0 + X_2 X_1$$

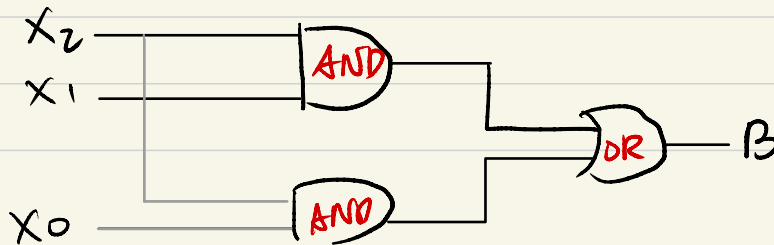

POS

A:

$x_1 x_0$	00	01	11	10
x_2				
0	0	0	0	0
1	1	1	1	1

$$A' = x_2'$$


$$A = x_2$$

B:

$x_1 x_0$	00	01	11	10
x_2				
0	0	0	0	0
1	0	1	1	1

$$B' = x_2' + x_1' x_0'$$
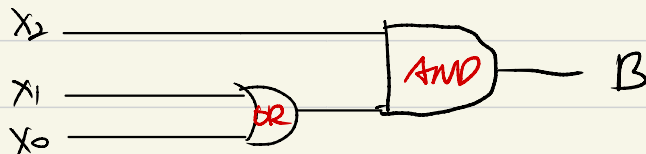
$$B = (x_2' + x_1' x_0')' = x_2 (x_1 + x_0)$$




Components needed for LAB II

Names	Amount
Solerless Breadboard	×1
74LS08 <i>AND</i>	×1
74LS32 <i>OR</i>	×1

74LS04

Connection Diagram

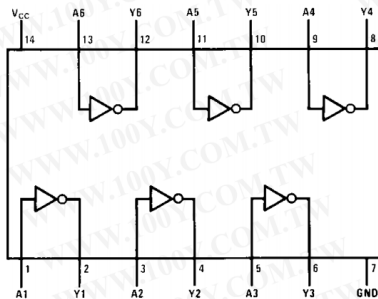

Function Table

$$Y = \overline{A}$$


Input	Output
A	Y
L	H
H	L

H = HIGH Logic Level

L = LOW Logic Level

74LS08

Connection Diagram

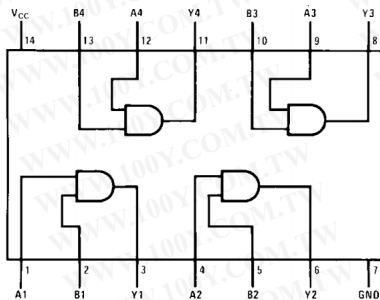

Function Table

$$Y = AB$$


Inputs		Output
A	B	Y
L	L	L
L	H	L
H	L	L
H	H	H

H = HIGH Logic Level

L = LOW Logic Level

74LS32

Connection Diagram

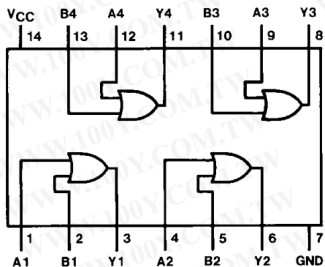

Function Table

$$Y = A + B$$

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H

H = HIGH Logic Level

L = LOW Logic Level