



Department of Computer Science and Information Engineering

National Cheng Kung University

數位系統實驗

陳培殷老師

國立成功大學 資訊工程系

Digital Integrated Circuit Design Laboratory





...
*Cheng
Kung
Univer
sity*

LAB - 02

陳培殷老師
國立成功大學 資訊工程系

*Di
git
al
In
te
gr
at*



Three representations for a circuit

1. Boolean Algebra


$$F_1 = x + yz$$

2. Truth

Table 真值表
n Input variables $\square 2^n$ combinations

Inputs

3. Circuit Diagram

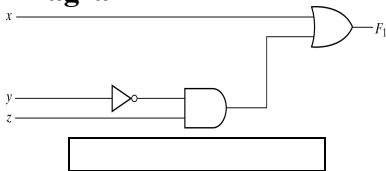

Equipment

Names	Amount
Solerless Breadboard	×1
74LS00	×1
74LS04	×1
74LS08	×1
74LS32	×1

Lab notice

- Input




- Output




Lab notice

Correct

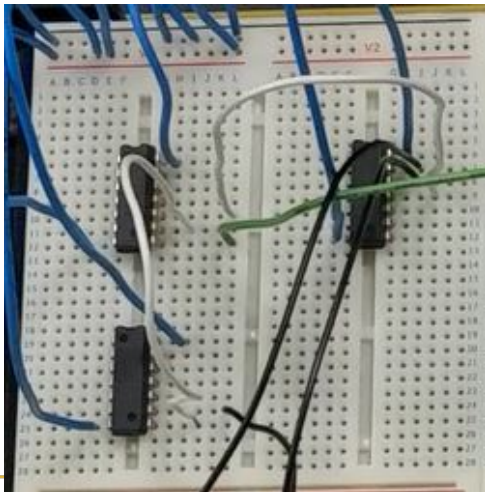

VCC : ●


GND : ●

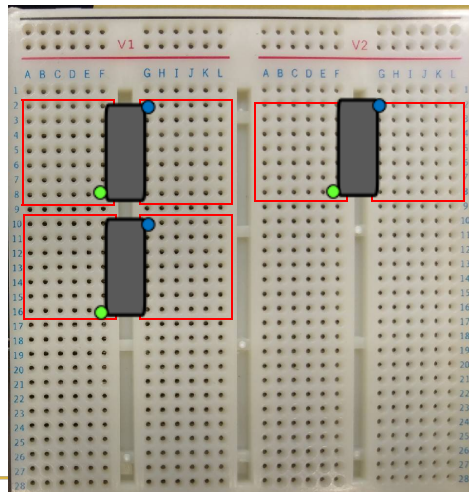


Lab notice

Wrong

a

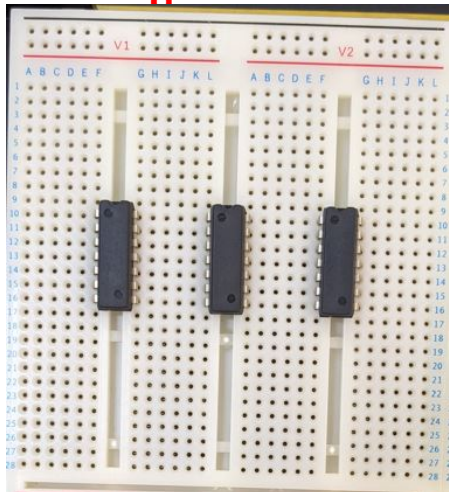


Overlap

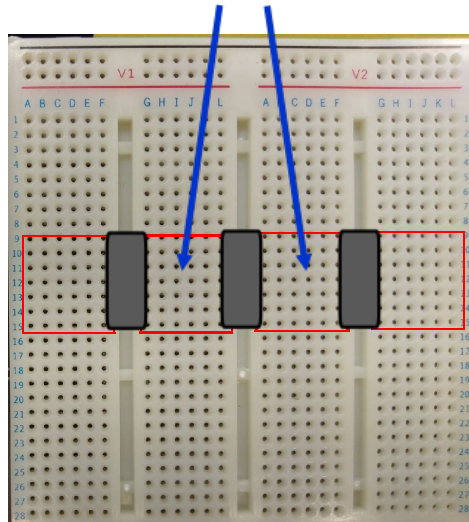


Lab notice

Correct

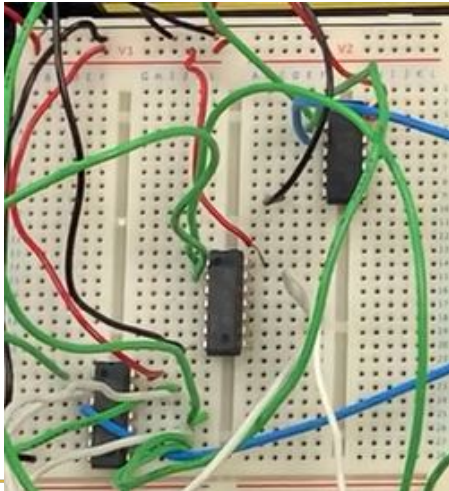


VCC : ●

GND : ●

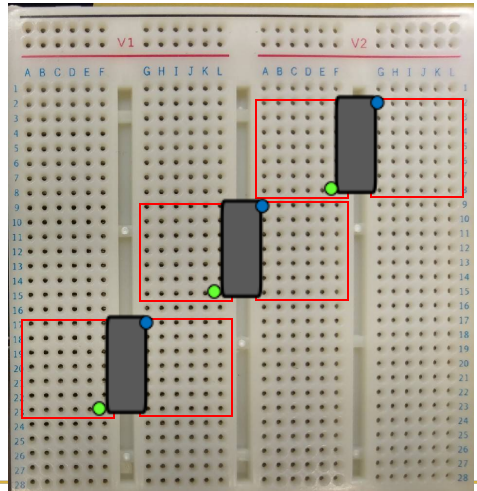


Lab notice

Correct



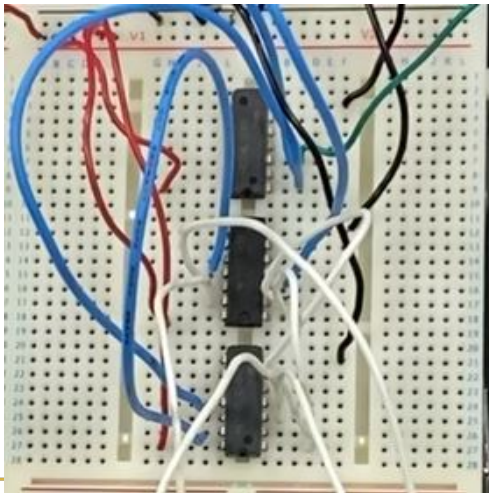


VCC : ●



GND : ●

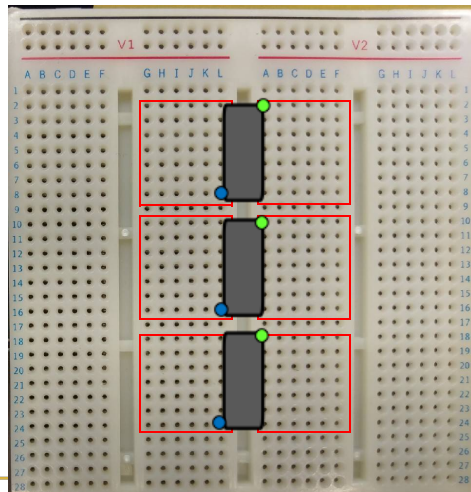

Lab notice

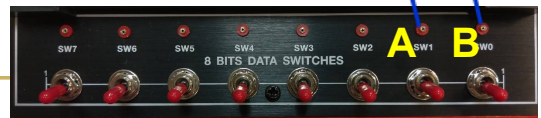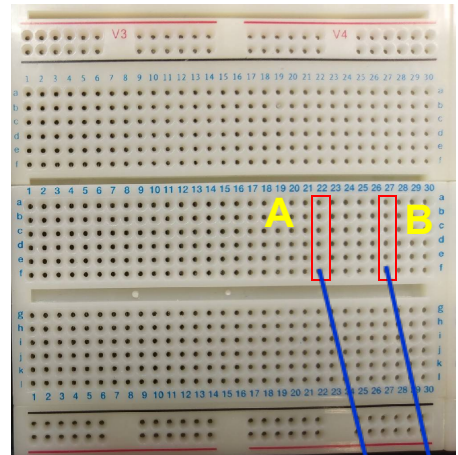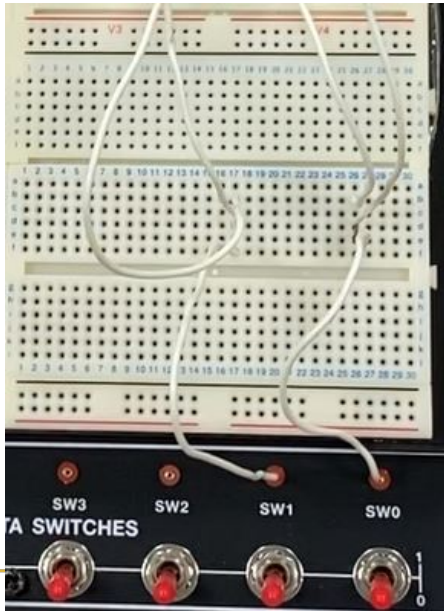

Lab notice

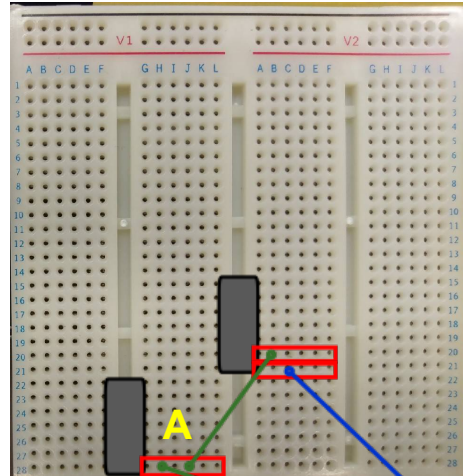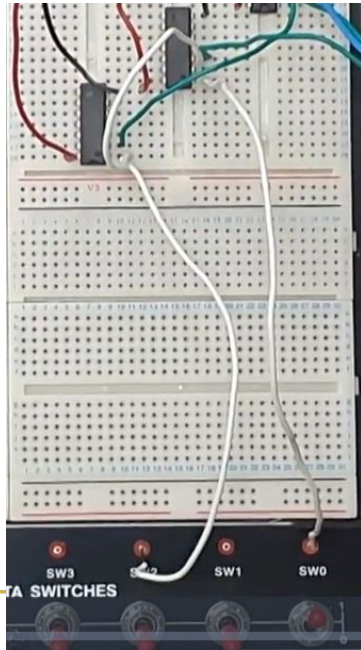

Lab 02_1

- Please draw their Truth Tables and implement the circuits with breadboard.

2-1-1 • $F1(A, B) = (A + B)'(A' + B')$

2-1-2 • $F2(A, B) = A' + AB$

A	B	F1
0	0	1
0	1	0
1	0	0
1	1	0

A	B	F2
0	0	1
0	1	1
1	0	0
1	1	1



Lab 02_2 - Half Adder (1/2)

- A half adder (HA) consists of two inputs (A and B) and two outputs (Sum and Carry). “A” denotes the summand and “B” is the addend. Sum and Carry mean the output sum and carry for input “A” and “B”. The truth table and Boolean algebra for the half adder are as follows.

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Carry} = A \cdot B$$

$$\text{Sum} = \overline{A} \cdot B + A \cdot \overline{B}$$


$$F(A, B) = A'B' + A'B + AB' + AB$$


Lab 02_2 - Half Adder (2/2)

Please

- (a) draw the circuit diagram of the half adder according to the truth table shown in previous page.**
 - (b) implement the circuit on the breadboard.**
-

Lab 02_3 – Comparator(1/2) 比較器

- There are two inputs denoted as A and B. Both A and B are 1-bit value. A comparator is designed to determine whether A is equal to B or not. The output results are represented with E .
- The function and truth table of the comparator is described as follows.

$$E = \begin{cases} 1 & , \text{if } A \text{ is equal to } B \\ 0 & , \text{else} \end{cases}$$

Lab 02_3 – Comparator(2/2)

Please

- (a) draw the truth table of the comparator.
- (b) draw the circuit diagram of the comparator.
- (c) implement the circuit on the breadboard.

A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

$$F(A, B) = (A'B') + (AB)$$

$$F(A, B) = A'B' + A'B + AB' + AB$$
