




LAB - 07

陳培殷老師

國立成功大學 資訊工程系

Sequential Circuit (1/3) 循序电路 { 同步, 非同步

 A sequential circuit is a system whose outputs at any time are determined from the present combination of inputs and the previous inputs or outputs.




- Sequential components contain memory elements
- The output values of sequential components depend on the input values and the values stored in the memory elements

Sequential Circuit (2/3)

```
1 module sequential_circuit(clk, reset);
2   input clk, reset;
3
4   always@(posedge clk or negedge reset)
5   begin
6
7       if(!reset)
8       begin
9           // Initialization
10        end
11        else
12        begin
13            // Circuit functionality
14        end
15    end
16 end
17
18 endmodule
19
```

正緣同步電路

低位準非同步重置

 

Sequential Circuit (3/3)

- Blocking statement vs nonblocking statement**

```
27 module combinational_circuit(in, a, b);
28
29 input in;
30 output reg [3:0] a,b;
31
32 input in;
33 output reg [3:0] a,b;
34
35 always@(*)
36 begin
37     if(in == 0)
38     begin
39         a = 4'h1;
40         b = 4'hf;
41
42         a = b; // a -> 4'hf
43         b = a; // b -> 4'hf
44     end
45 else
46     begin
47         a = 4'h1;
48         b = 4'hf;
49
50         b = a; // b -> 4'h1
51         a = b; // a -> 4'h1
52     end
53 end
54
55 end
56
57 endmodule
```

```
1 module sequential_circuit(clk, reset);
2 input clk, reset;
3
4 reg [3:0] a,b;
5
6 always@(posedge clk or negedge reset)
7 begin
8
9     if(!reset)
10    begin
11        a <= 4'h1;
12        b <= 4'hf;
13    end
14 else
15    begin
16        a <= b; // a -> 4'hf
17        b <= a; // b -> 4'h1
18    end
19
20 end
21
22 endmodule
```

Lab I (1/3)

- 請設計一個具備下列功能的計數器：

- 正緣同步電路，低位準非同步重置
- 當reset訊號為0，將目前狀態暫停，輸出維持0
- 當reset訊號為1

1) Up_Down = 0 ， 每秒計數減1

- EX : 0 -> F -> E -> -> 2 -> 1 -> 0 -> F

2) Up_Down = 1 ， 每秒計數加1


- EX : 0 -> 1 -> 2 -> -> E -> F -> 0 -> 1

- FPGA版之clock頻率為50MHz，需藉由除頻器將clock訊號降為1Hz

- 實現方式為透過一個計數器，計算經過幾個時脈正緣，當計數到 50×10^6 即代表經過一秒
-

Lab I (2/3)

 - 請將計數的數值顯示於七段顯示器
- 系統架構圖請參考下方
 - Input : clock(**CLOCK_50**) , reset(SW0), Up_Down(SW1)
 - Output : out(7 bits , HEX06~HEX00)
- 可使用structural description設計，其中，除頻器及計數模組為循序電路，七段顯示器控制模組則為組合電路




Lab I (3/3)

- 輸出範例

1) Up_Down = 0



1) Up_Down = 1

 

Lab - Hint(1/2)

- **Frequency Divider (sequential circuit)**
 - 將clock頻率從50MHz降為1Hz
- **Counter (sequential circuit)**
 - 每秒進行計數
- **Seven Display (combinational circuit)**
 - 將Counter數值轉為七段顯示器控制訊號
- **Module呼叫範例 (Structural description)**
 - **FrequencyDivider** u_FreqDiv (.clk(clock), .reset(reset), .clk_div(clock_div));
 - **Counter** u_counter(.clk(clock_div), .reset(reset), .count(count));
 - **SevenDisplay** u_display(.count(count), .out(out));

```
module_name unit_name(.port_name(signal_name),.port_name(signal_name).....)
```

Lab – Hint(2/2)

- 除頻器範例：
 - 每0.5秒改變一次訊號(div_clk)

```
1  `define TimeExpire 32'd25000000
2
3  module clk_div(clk,rst,div_clk);
4  input  clk,rst;
5  output div_clk;
6
7  reg div_clk;
8  reg [31:0]count;
9
10 always@(posedge clk)
11 begin
12     if(!rst)  低位準同步reset
13     begin
14         count <= 32'd0;
15         div_clk <= 1'b0;
16     end
17     else
18     begin
19         if(count == `TimeExpire)
20         begin
21             count <= 32'd0;
22             div_clk <= ~div_clk;
23         end
24         else
25         begin
26             count <= count + 32'd1;
27         end
28     end
29 end
30
31 endmodule
```

Notice

- 請勿命名中文或數字開頭的資料夾
- Device family 請確認與 FPGA Chip 符合 (5CEFA4F23C7)
- Top module name & Project name 需要一致
- 在組合電路中，case、if...else...若沒有寫滿，合成後會產生latch